
 

 
## Time constraints for digital circuits

A quick note about the time constraints associated with flip-flops and combinatorial circuits.




Input constraints for a flip-flop:

- $t_{setup}$  (“Setup Time”) is the time **before** the rising edge of the clock CLK during which the **D** input should remain stable (i.e. not changing).
- $t_{hold}$  (“Hold Time”) is the time **after** the rising edge of the clock CLK during which the **D** input should not change.
- $t_a$  is the time window where input **D** must be stable ( $t_a = t_{setup} + t_{hold}$ ).

Output constraints for a flip-flop:

 
- $t_{ccq}$  (“min CLK to Q delay”) is the time **after** the rising edge of CLK at which the **Q** output would be unstable (i.e. could change).
- $t_{pcq}$  (“max CLK to Q delay”) is the time **after** the rising edge of CLK at which the **Q** output is guaranteed to be stable.



Minimum and maximum delays for combinatorial circuits:


Combinational circuits also have timing constraints for the logic gates. The “min delay”  $t_{cd}$  for a circuit (in green) is the minimum time between the moment an input of the circuit changes and the moment the output of that circuit begins to change.

 The “max delay”  $t_{pd}$  (in red) is the maximum time between when an input to the circuit changes and when the output of that circuit stabilises.



Timing constraints for flip-flops and combinational circuits:

 The following diagram shows a circuit for some combinational logic between two flip-flops. Here, the input **D2** of flip-flop **R2** comes from the output **Q1** of flip-flop **R1** after passing through the combinational circuit **CL**.




Thus, the output of the **R1\_CL** circuit (i.e. **D2**) must be stable for a combined minimum duration greater than or equal to the setup time  $t_{setup}$  of the **R2** flip-flop if we want the latter to be able to "see" the new value **D2**. This value must also remain unchanged for a duration  $t_{hold}$  after the rising edge of the clock so that the **R2** flip-flop has enough time to make a copy.

To respect the constraint on  $t_{hold}$ , we have:


$$t_{hold} < \min\_delay(flip-flop) + \min\_delay(CL) < t_{ccq} + t_{cd}$$

and to respect the constraint on  $t_{setup}$ :
 
$$T_c \geq \max\_delay(flip-flop) + \max\_delay(CL) + t_{setup} \geq t_{pcq} + t_{pd} + t_{setup}$$



**Example:**

 

**Timing specifications:**

*Flip-flops*

$$t_{ccq} = 30 \text{ ps}, t_{pcq} = 50 \text{ ps}$$

$$t_{setup} = 60 \text{ ps}, t_{hold} = 70 \text{ ps}$$

*Combinatorial components*

$$t_{pd} = 35 \text{ ps}, t_{cd} = 50 \text{ ps}$$

$$t_{pd} \text{ circuit} = 3 \times 35 \text{ ps} = 105 \text{ ps}$$

$$t_{cd} \text{ circuit} = 2 \times 25 \text{ ps} = 50 \text{ ps}$$

*Constraint on  $t_{setup}$*

$$T_c \geq (50 + 105 + 60) \text{ ps} = 215 \text{ ps}$$

$$f_c = 1/T_c \leq 4.65 \text{ GHz}$$

*Constraint on  $t_{hold}$*

$$t_{ccq} + t_{cd} > t_{hold}$$

$$(30 + 50) \text{ ps} > 70 \text{ ps} \text{ **verified!**}$$